

ESE 370: CIRCUIT-LEVEL OPTIMIZATION FOR DIGITAL
SYSTEMS

Project 2 Milestone: FIFO Queue

Mauricio Mutai, Jack Harkins

Instructor: Dr. Tania Khanna

TA: Martin Deng

Date: 11/26/16

December 12, 2016

Design Schematics

Top-Level Design

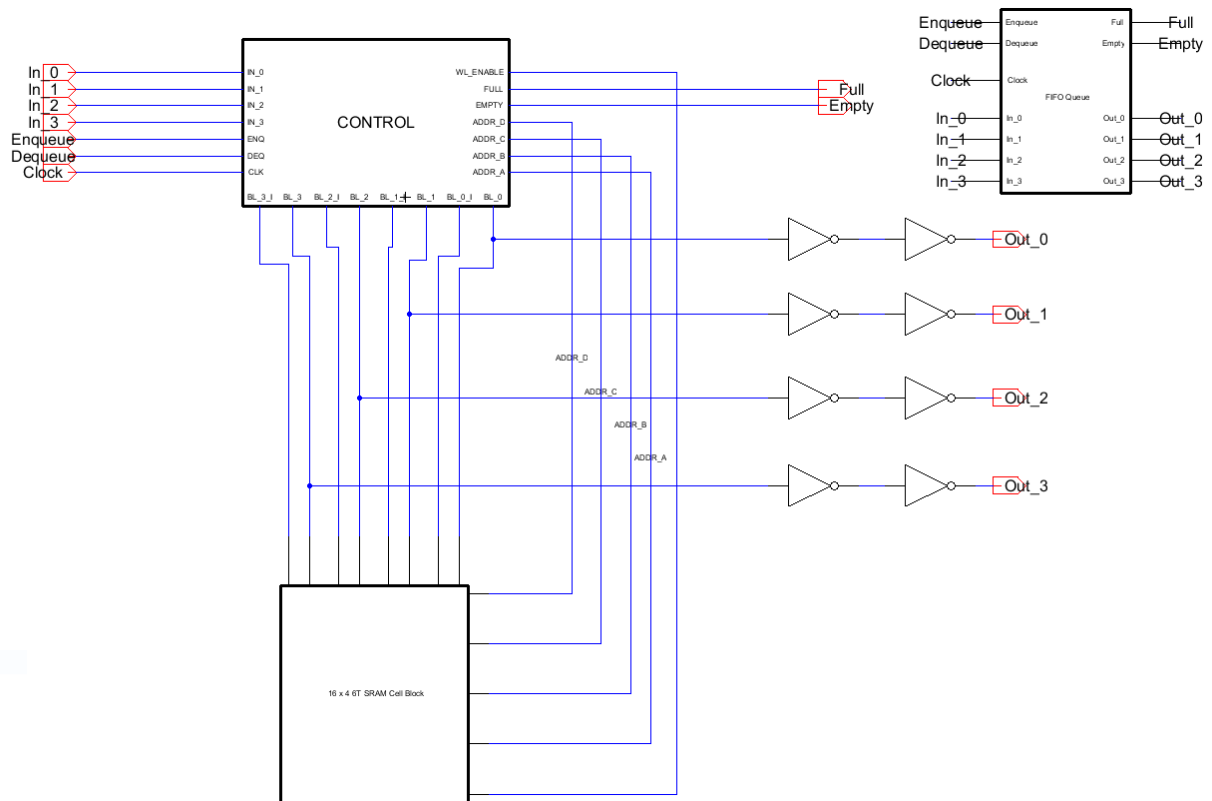


Figure 1: Queue top-level schematic

Memory Cell Block

 


Figure 2: Memory block toplevel schematic

 


Figure 3: Memory block schematic in detail, decoder

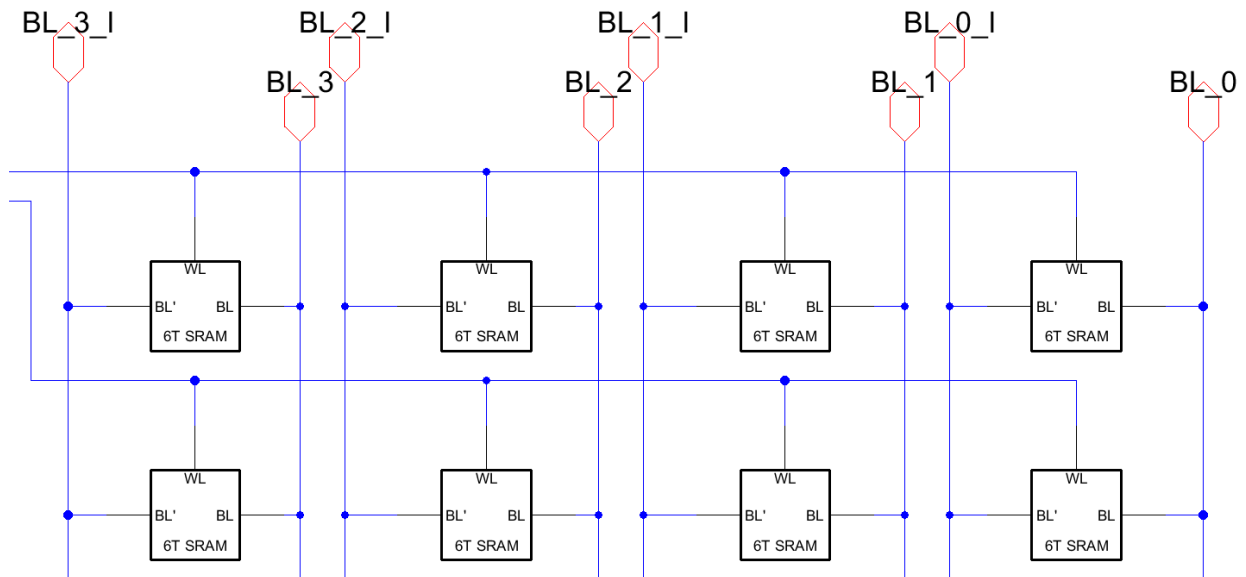


Figure 4: Memory block schematic in detail, word slice

6T SRAM Cell

 


Figure 5: SRAM cell schematic

Control Block

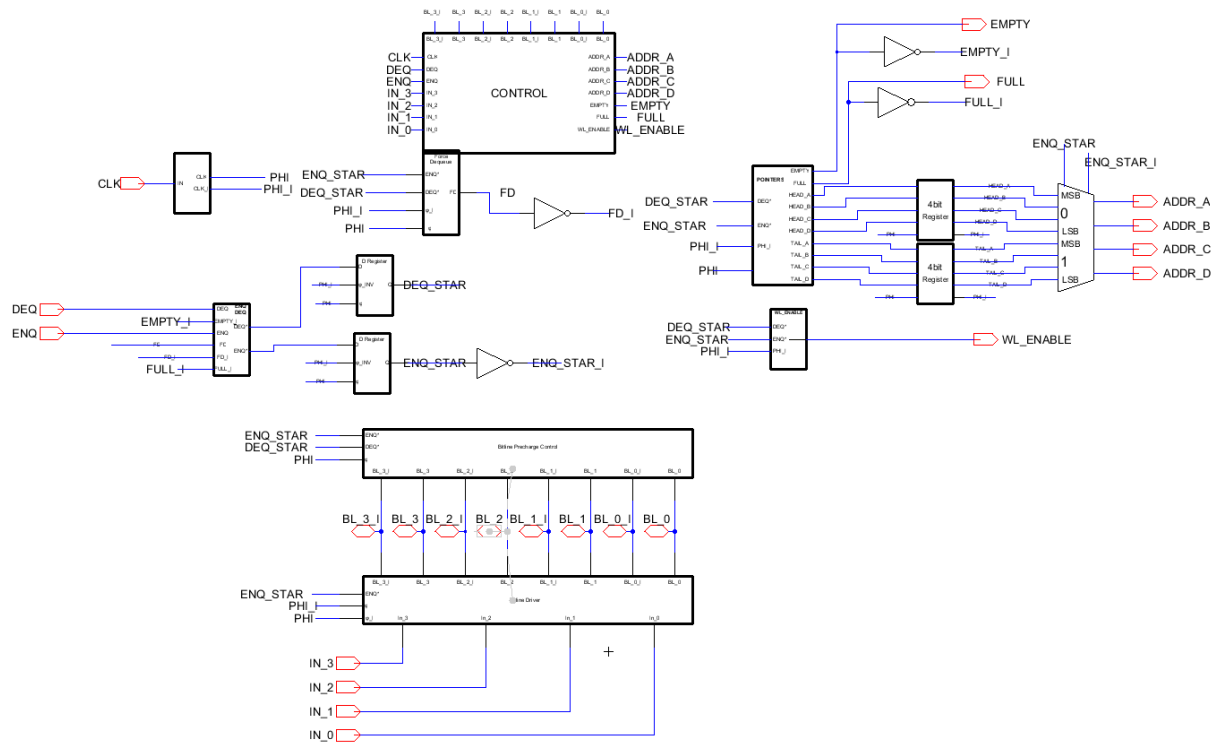


Figure 6: Control block toplevel schematic

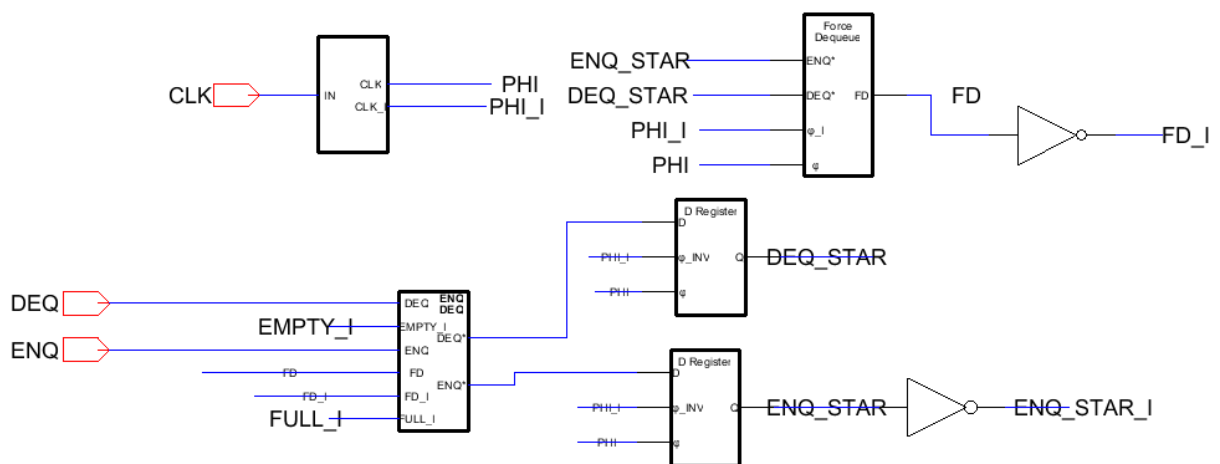


Figure 7: Control block schematic in detail, FD, clock generator, and ENQ*/DEQ* generation

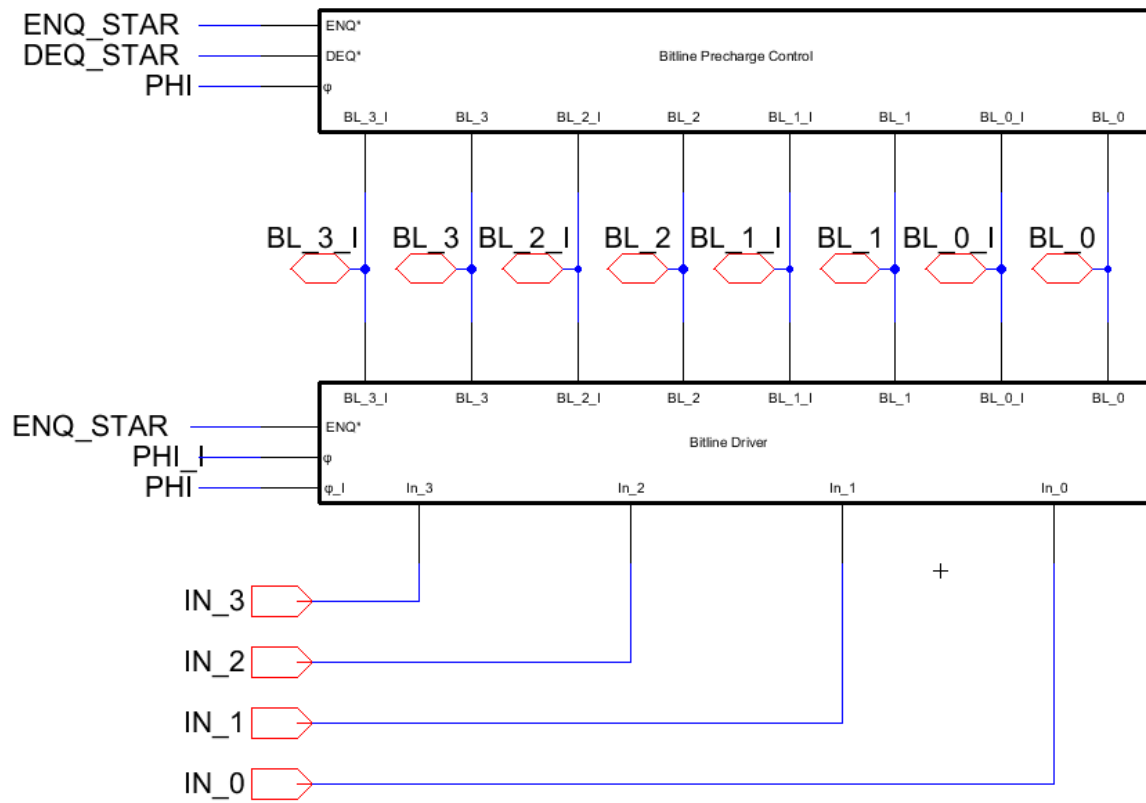


Figure 8: Control block schematic in detail, bitline driver and precharger

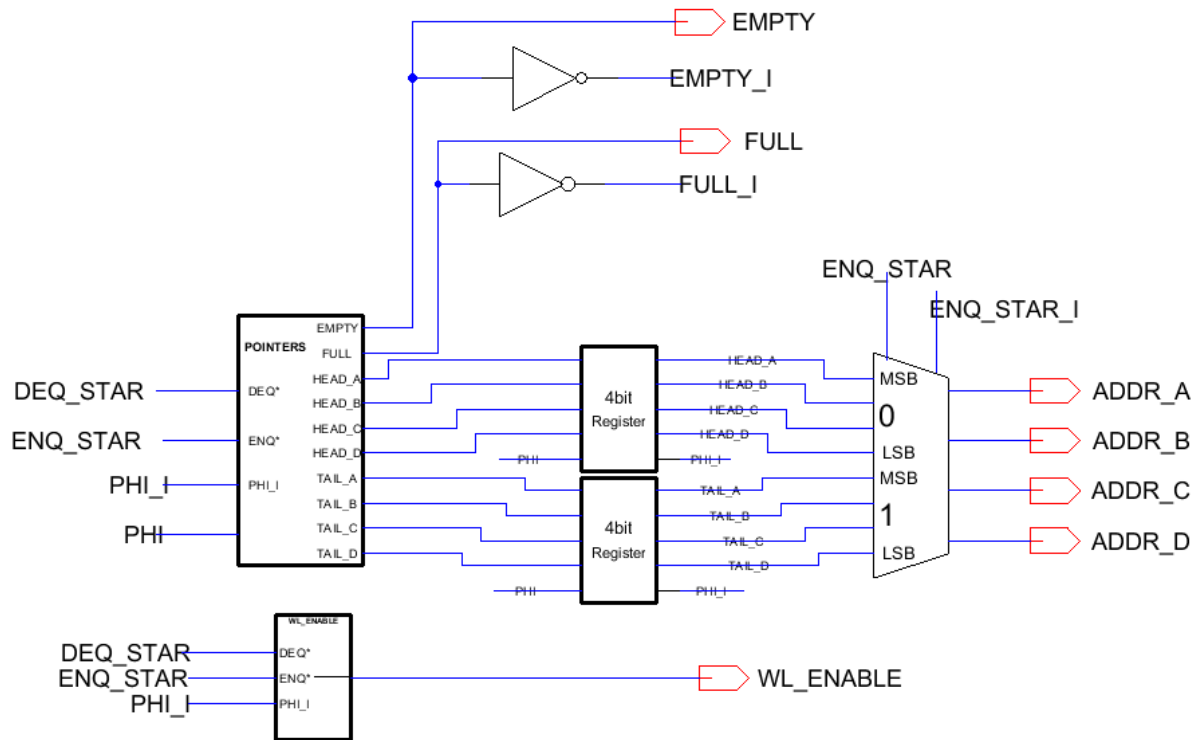


Figure 9: Control block schematic in detail, pointers, WL_EN, and EMPTY/FULL generation

Clock Generator

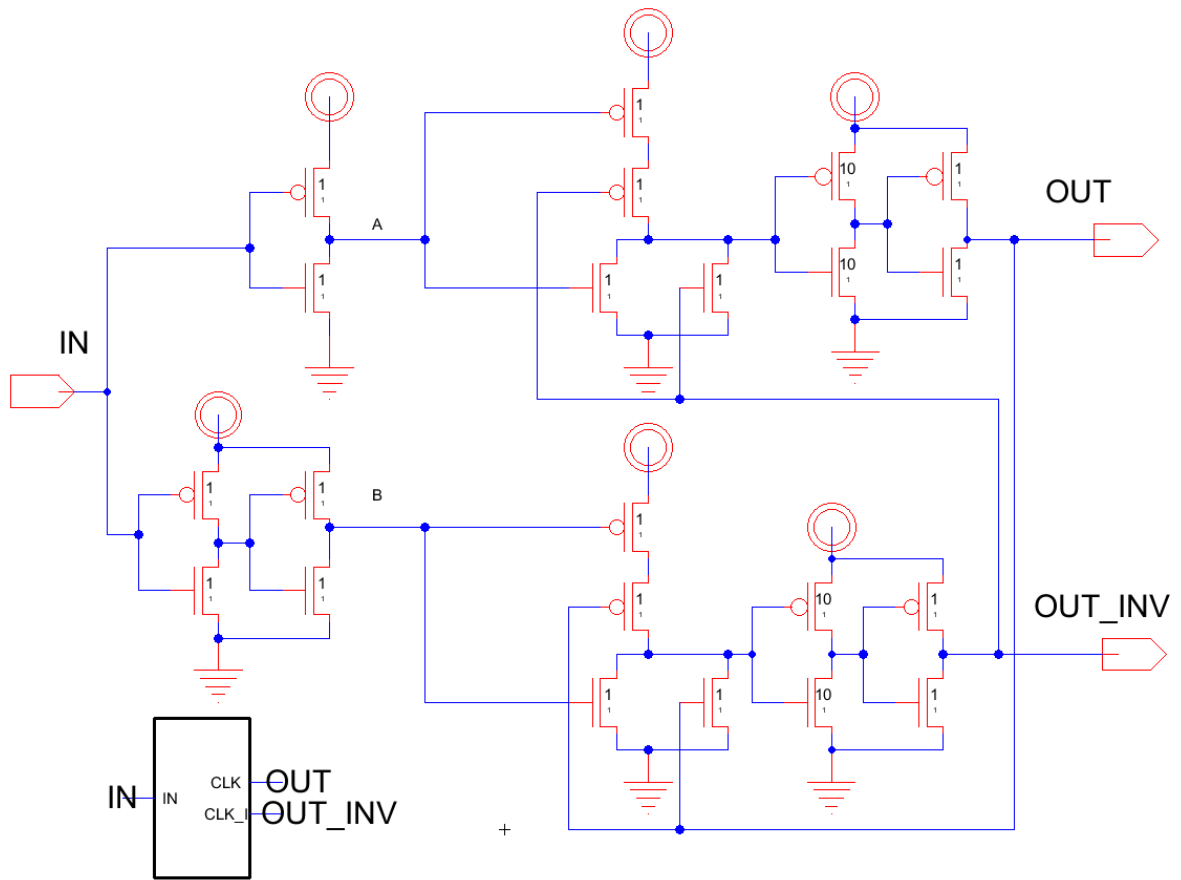


Figure 10: Clock generator schematic

Force Dequeue (FD)

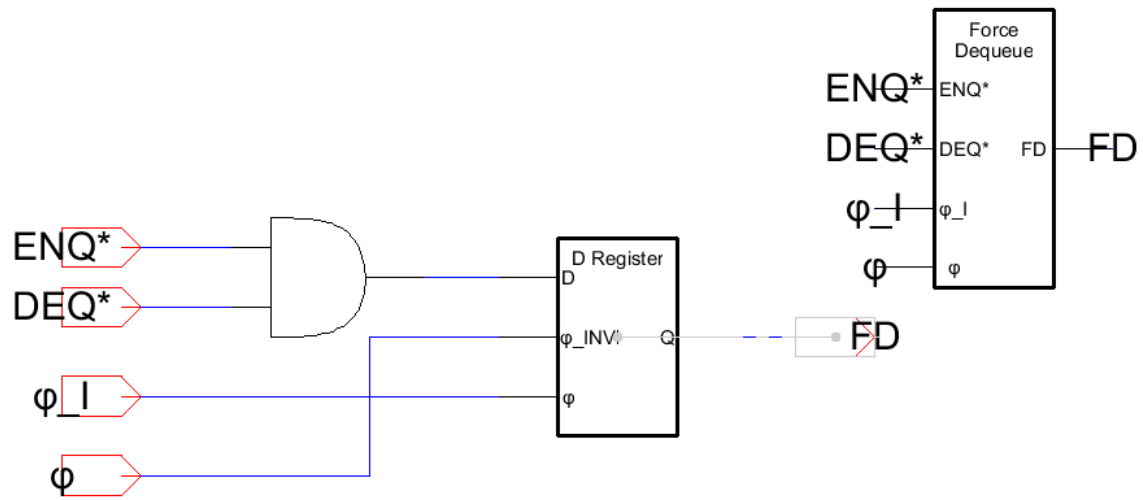


Figure 11: Force dequeue generation schematic

Pointers

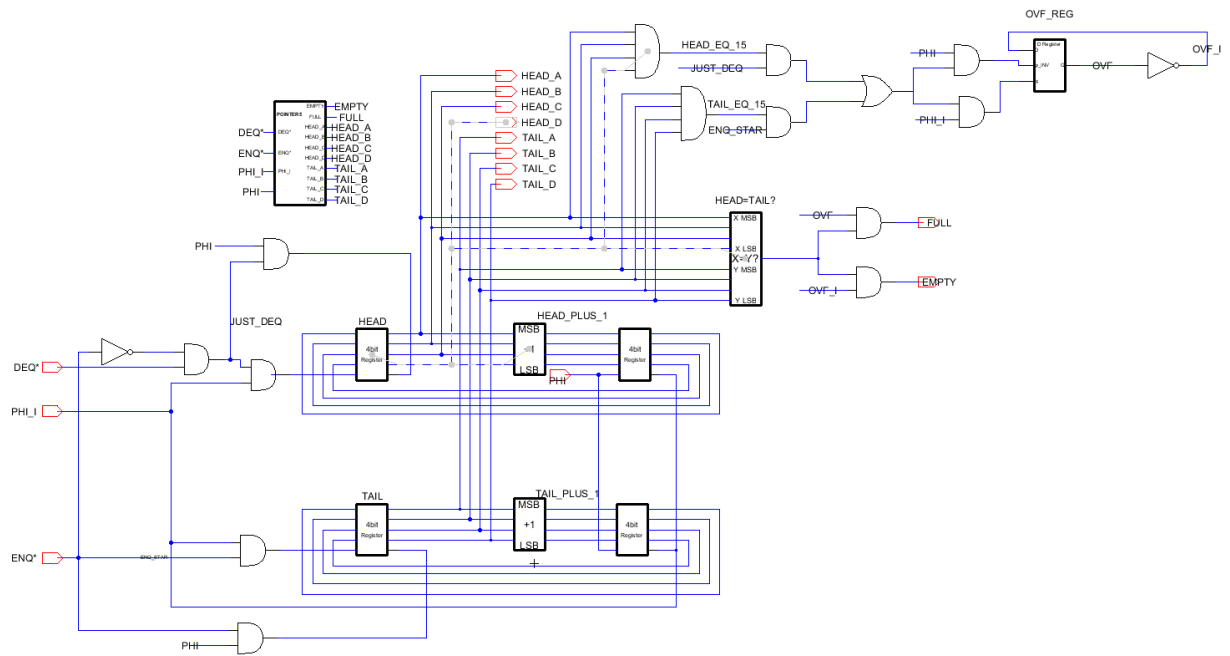


Figure 12: Pointers toplevel schematic

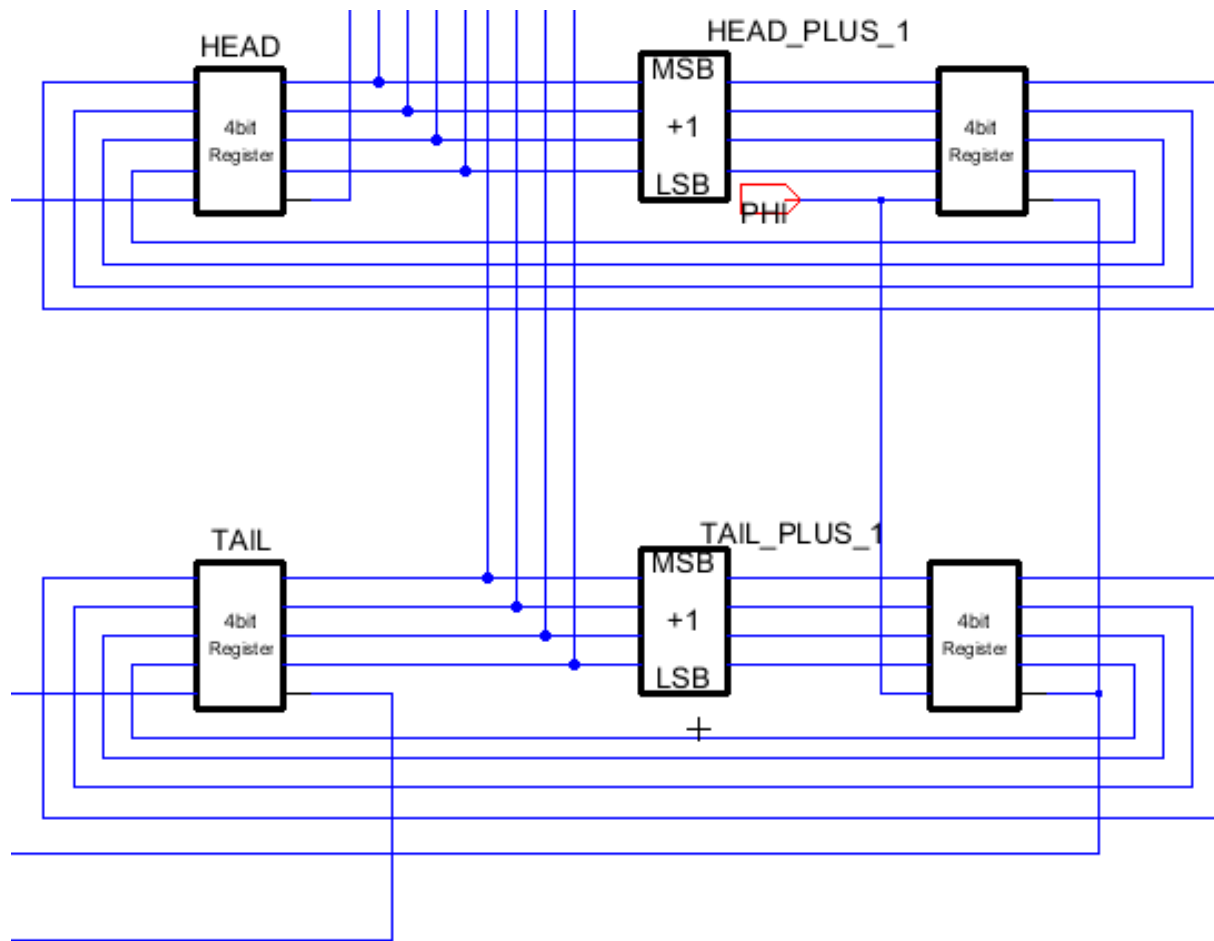


Figure 13: Pointers schematic in detail, head/tail state

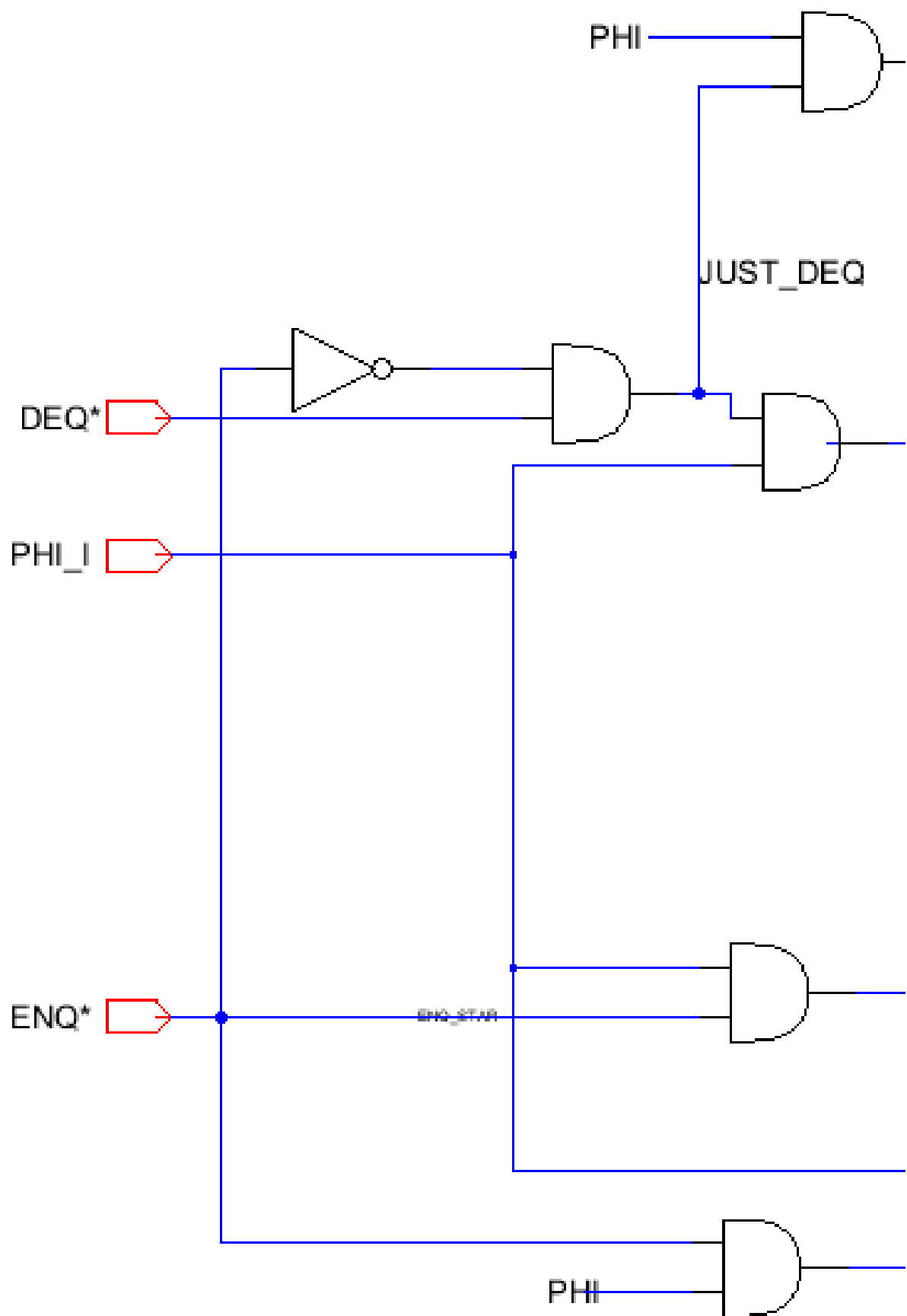


Figure 14: Pointers schematic in detail, inputs

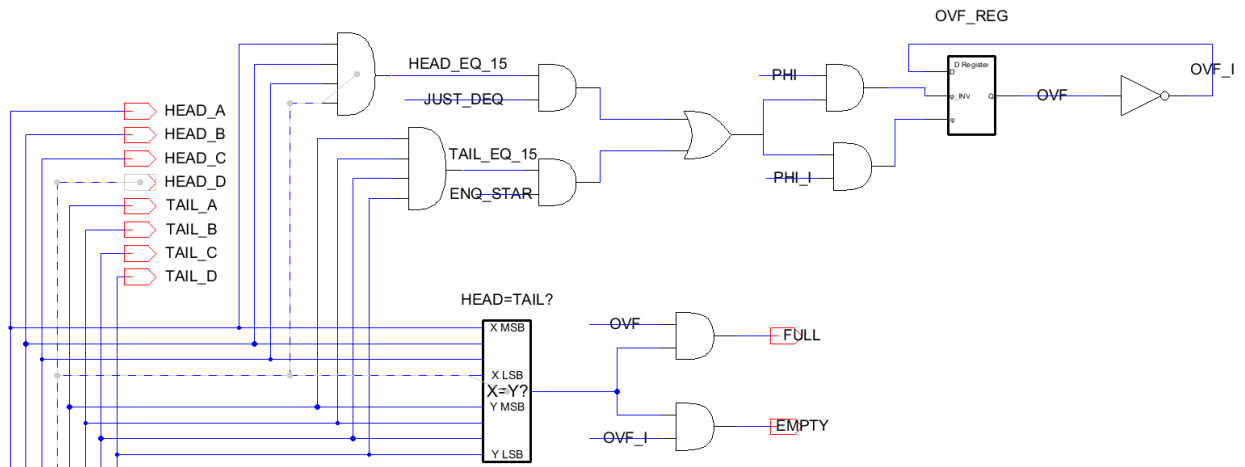


Figure 15: Pointers schematic in detail, overflow handler

D Latch

 


Figure 16: D latch schematic

D Register

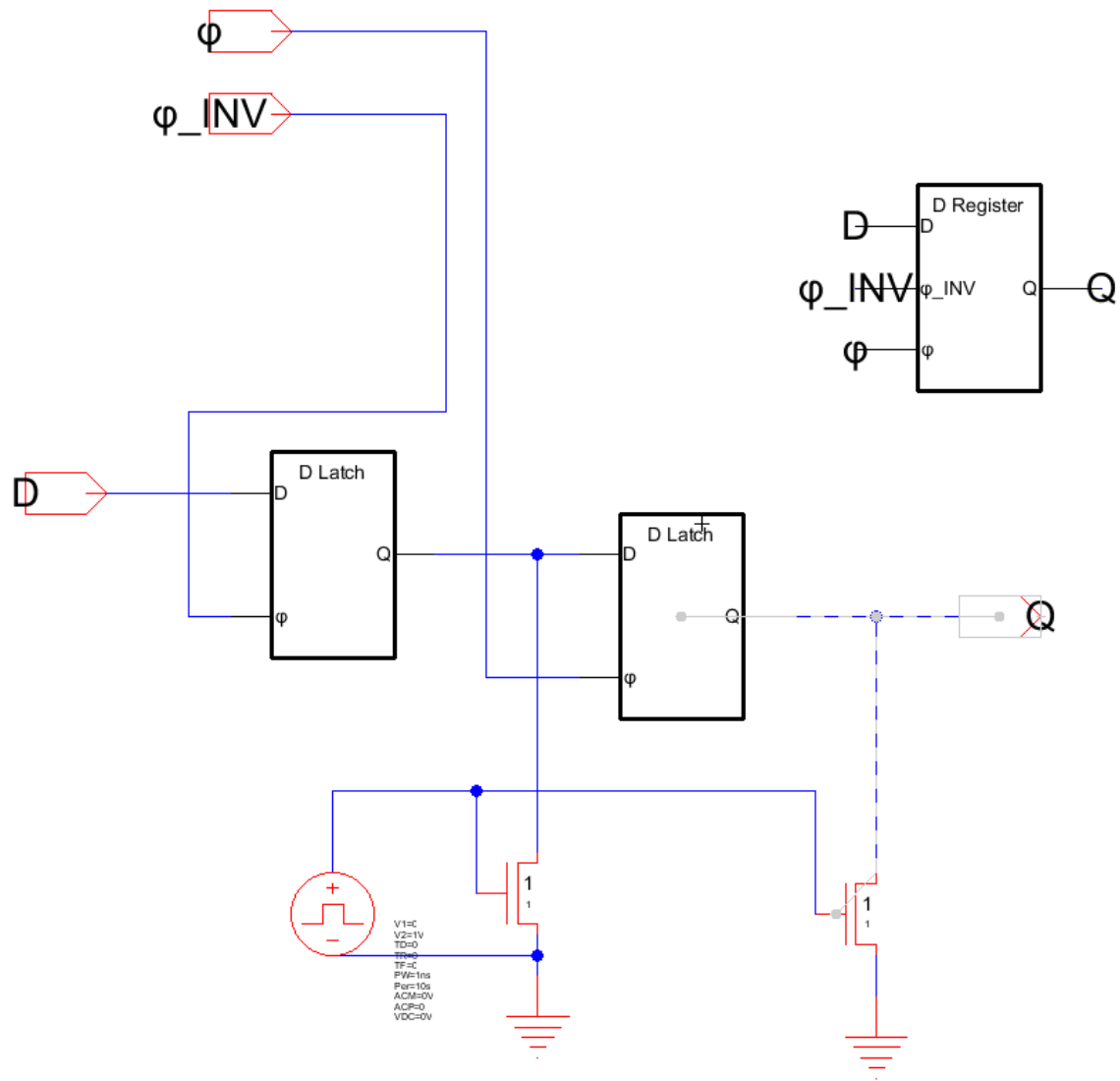


Figure 17: D register schematic

4-bit Register

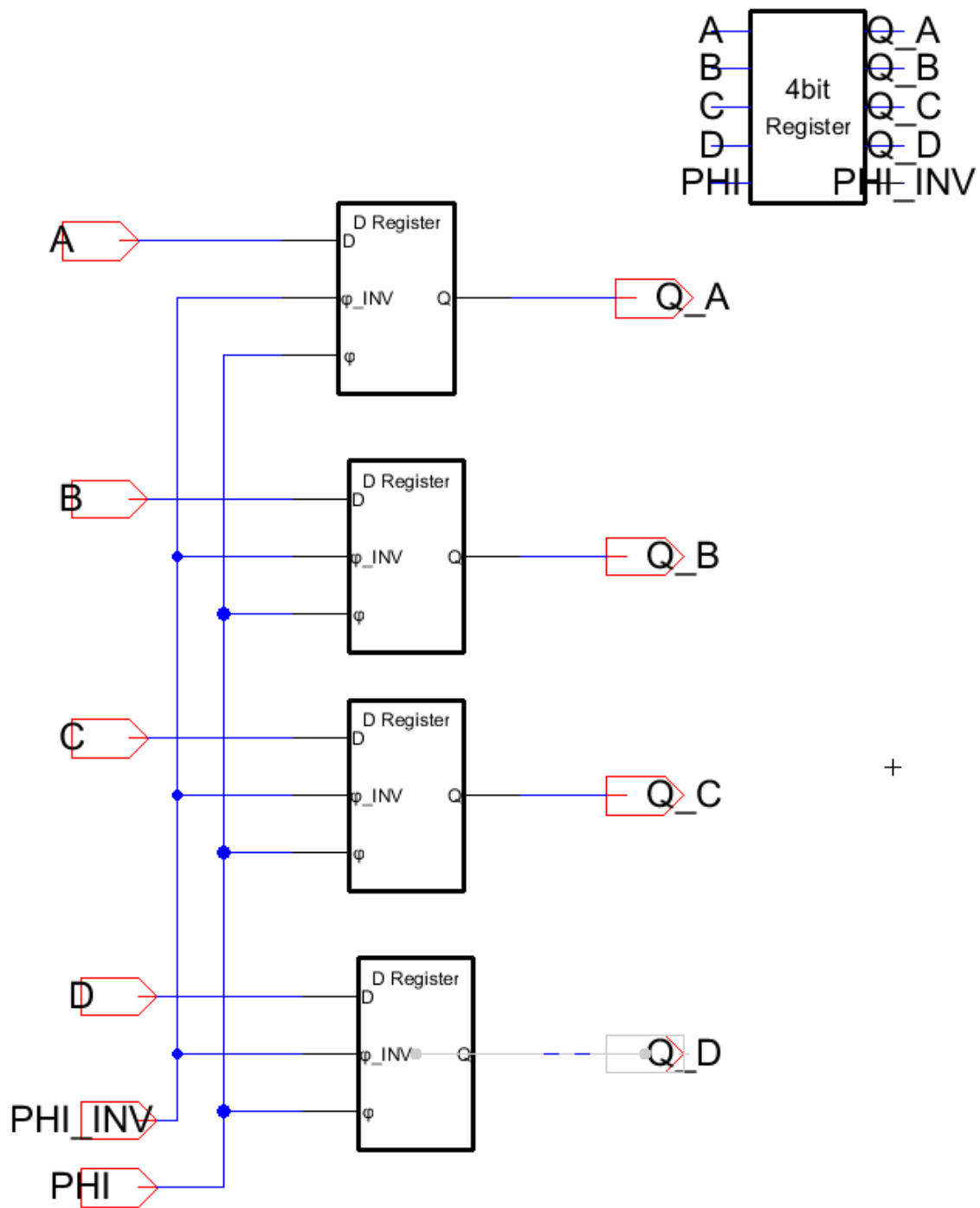


Figure 18: 4-bit register schematic

Incrementer

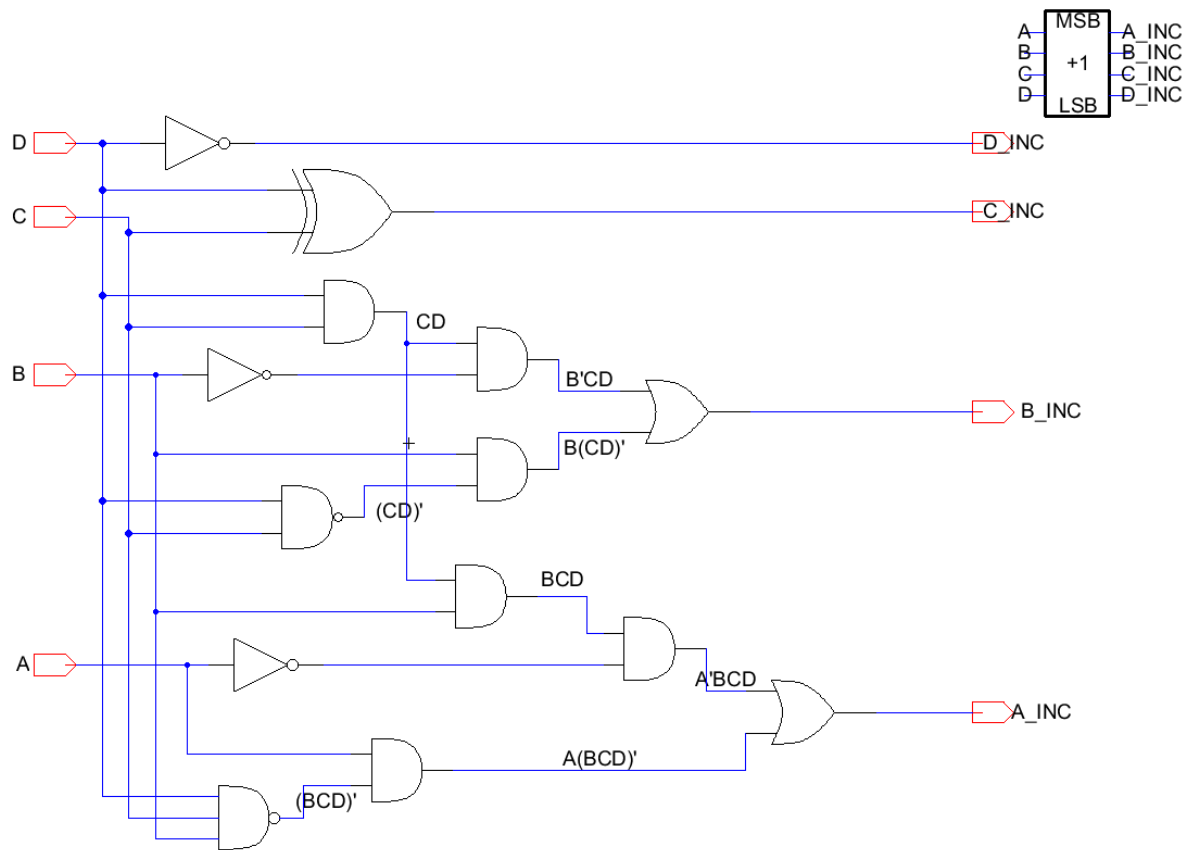


Figure 19: Incrementer schematic

Comparator

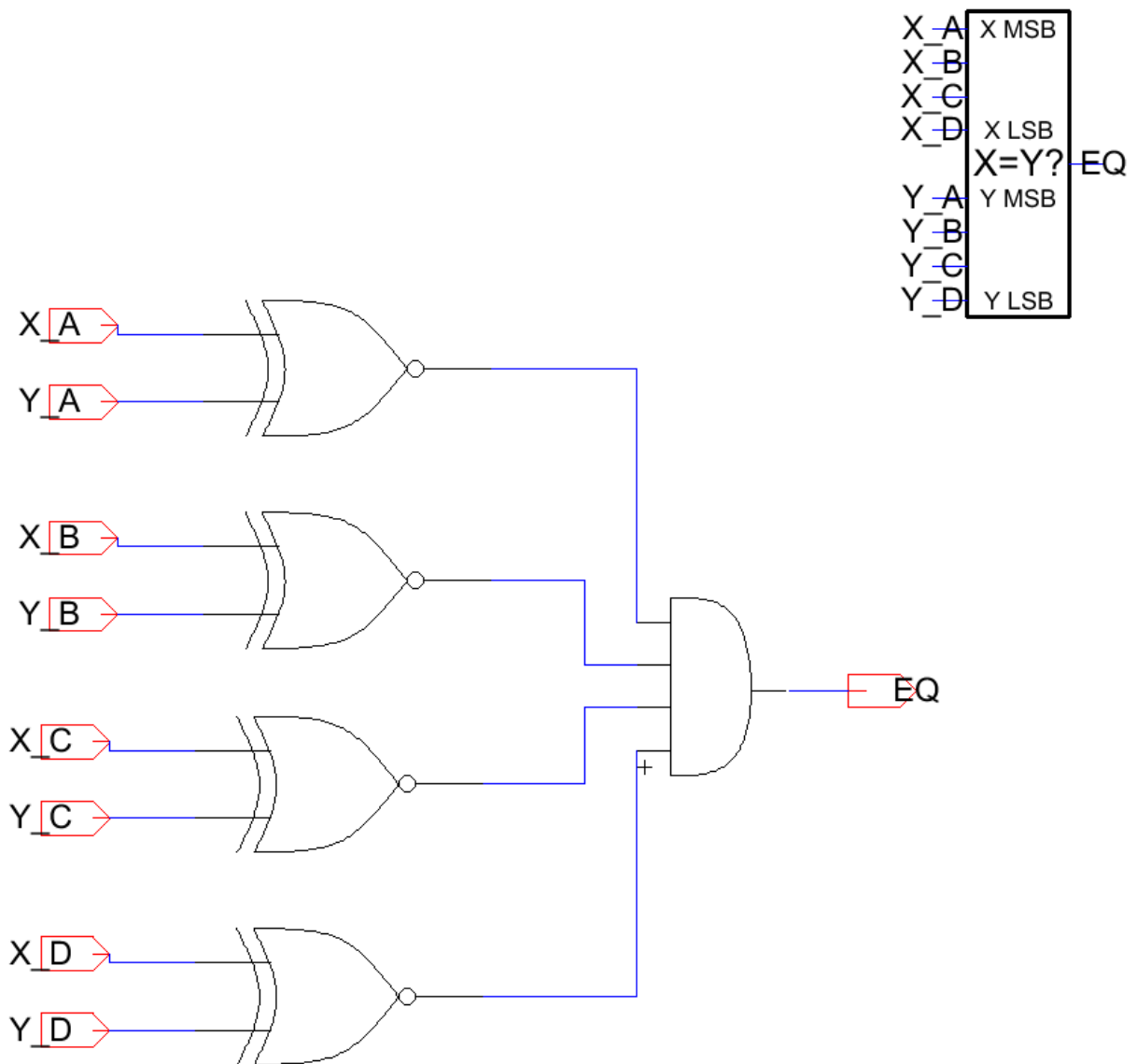


Figure 20: Equality comparator schematic

Mux

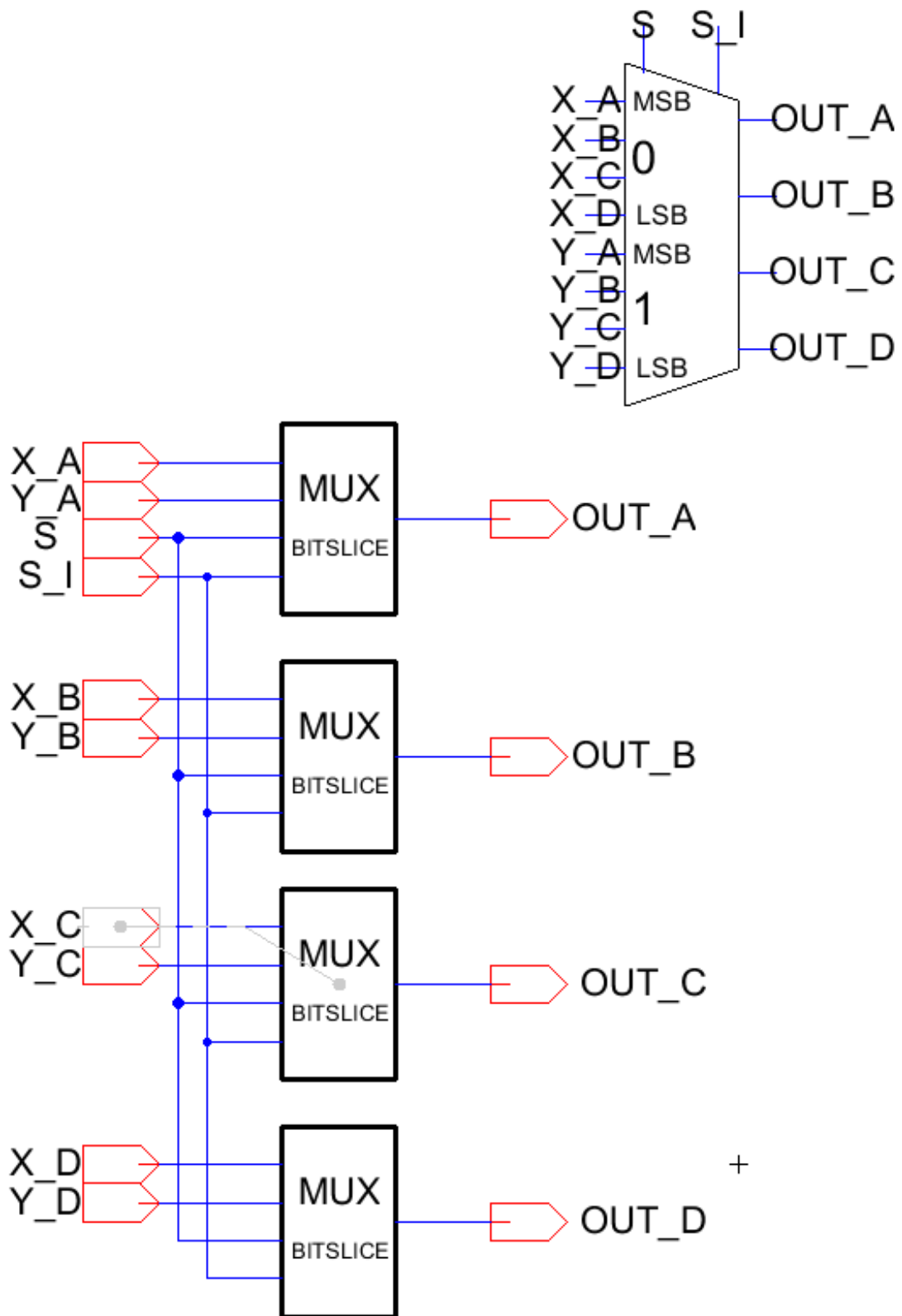


Figure 21: Mux schematic

Mux Bitslice

 


Figure 22: Mux bitslice schematic

Wordline Enable (WL_EN)

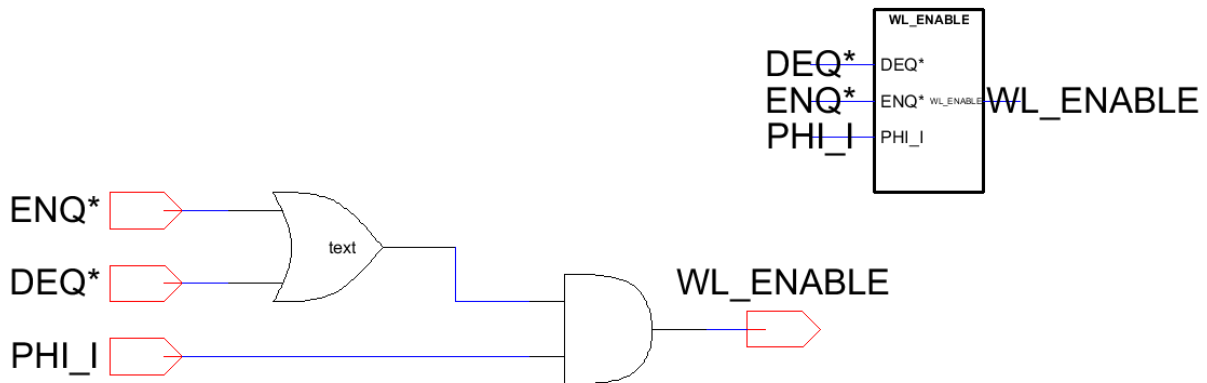


Figure 23: Word line enable generator schematic

ENQ*/DEQ* Generator

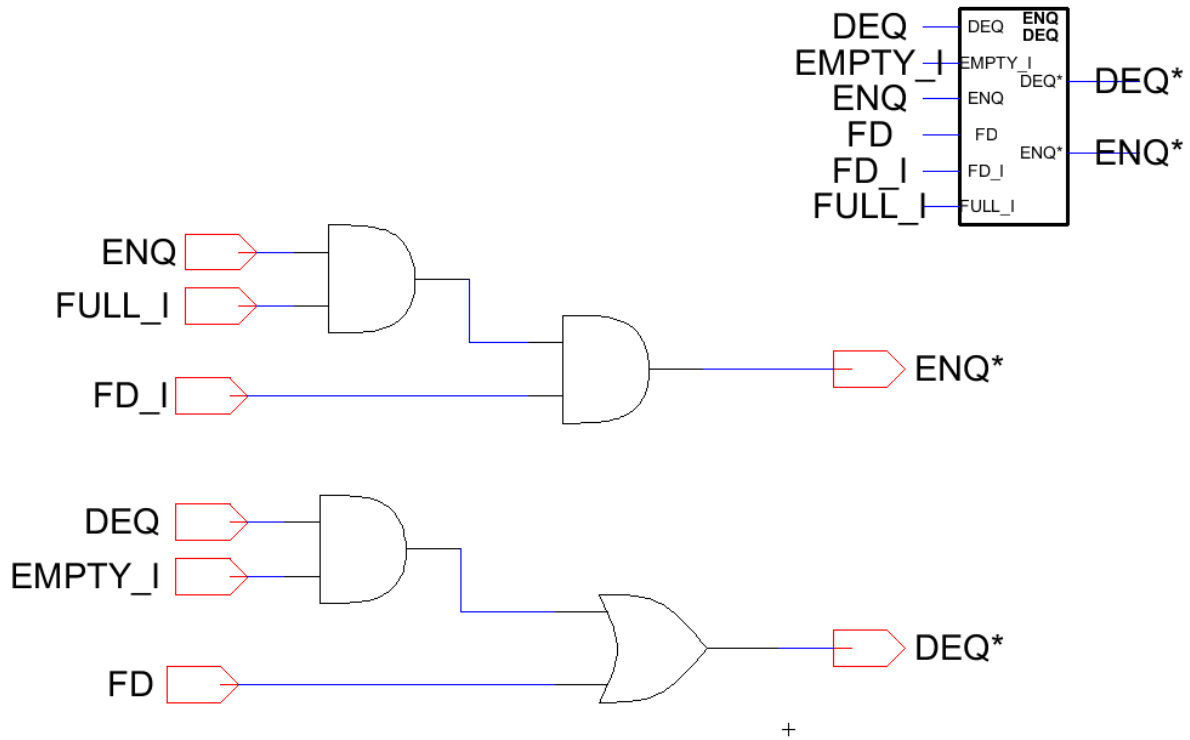


Figure 24: ENQ*/DEQ* generator schematic

4-bit Bitline Precharger

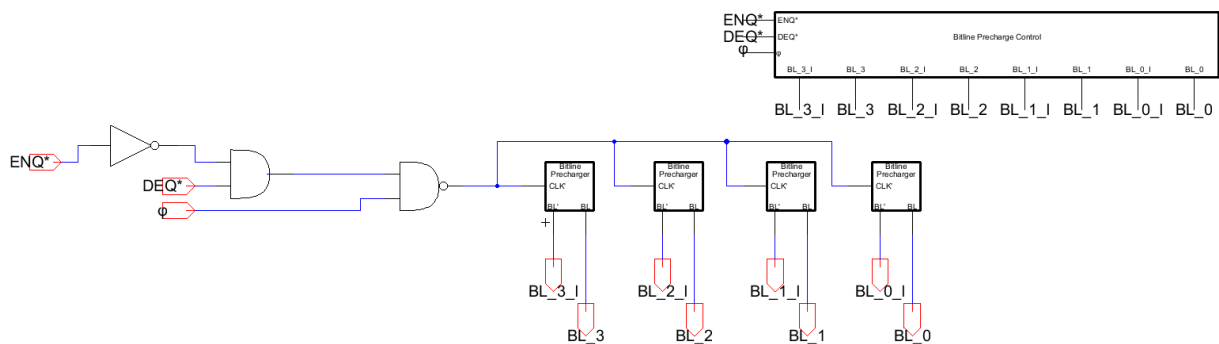


Figure 25: 4-bit bitline precharger schematic

1-bit Bitline Precharger

 


Figure 26: 1-bit bitline precharger schematic

Bitline Driver

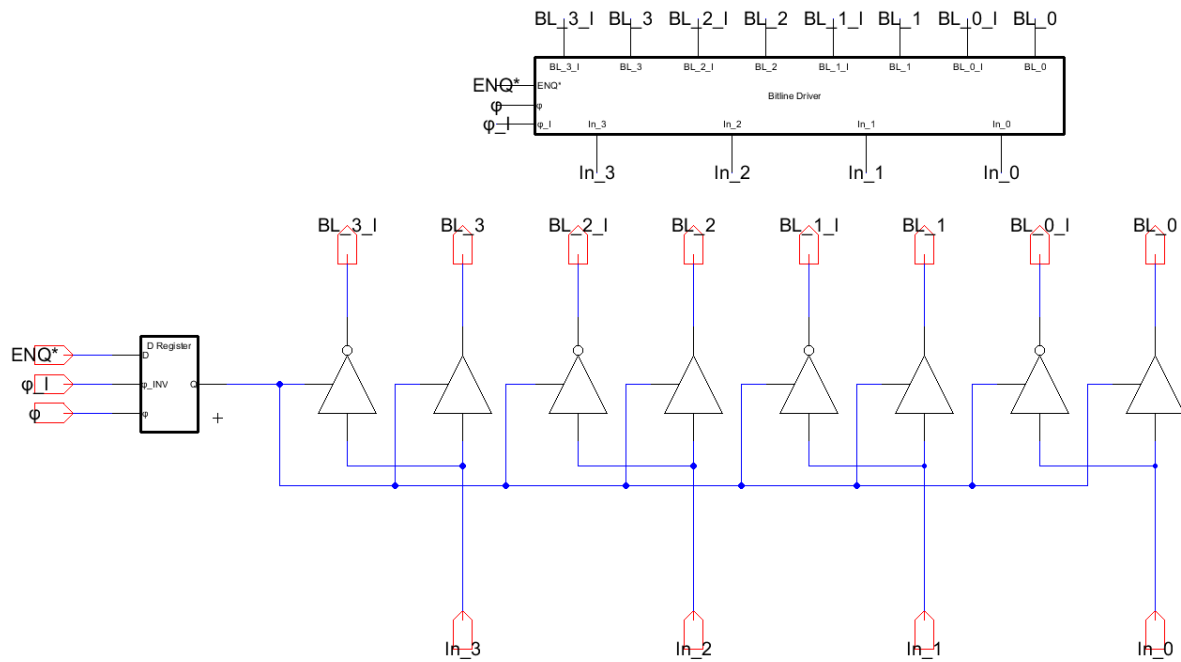


Figure 27: Bitline driver schematic

Inverter

 


Figure 28: Inverter schematic

NAND2

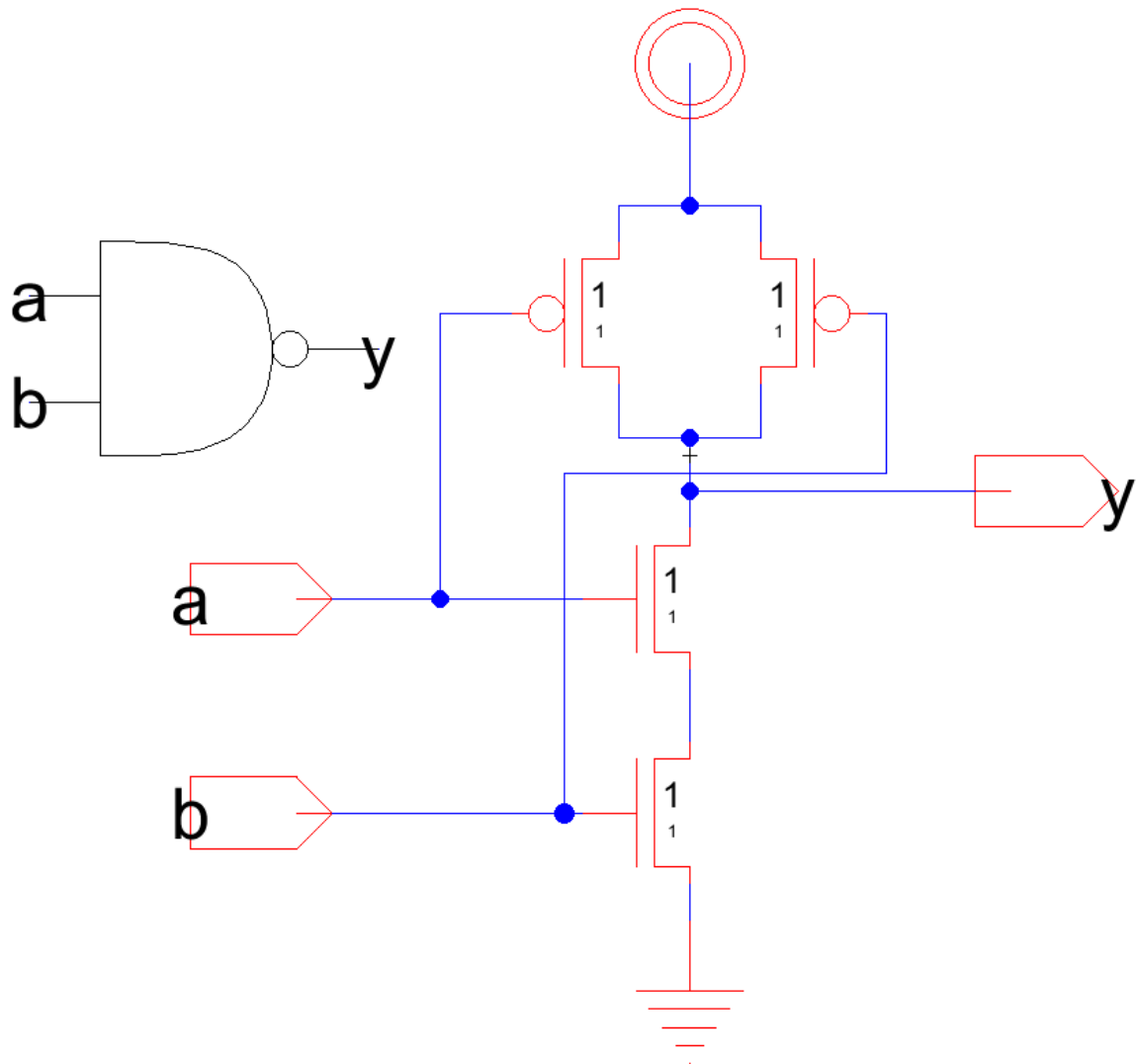


Figure 29: NAND2 gate schematic

AND2

 


Figure 30: AND2 gate schematic

AND4

 


Figure 31: AND4 gate schematic

NOR2

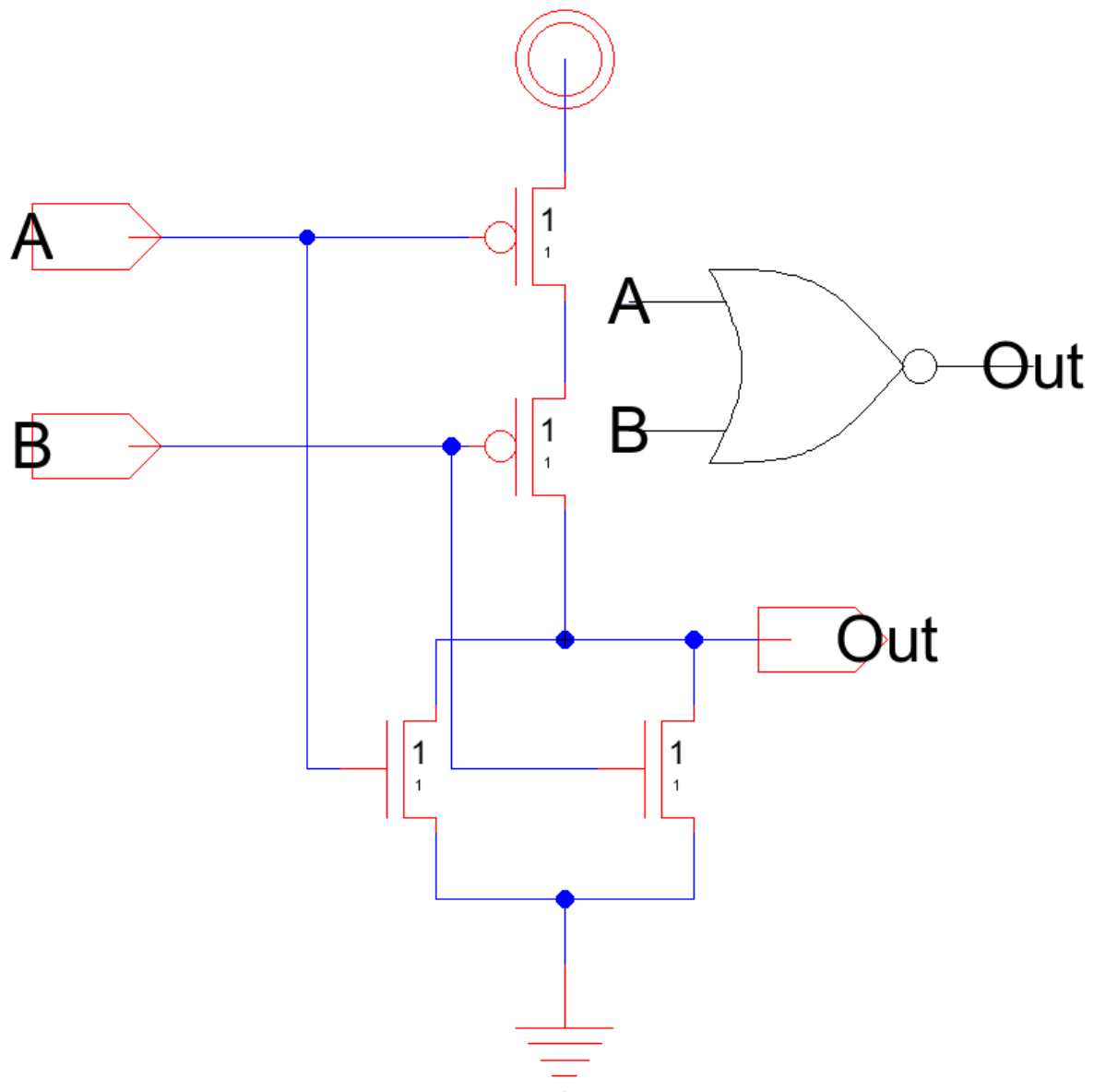


Figure 32: NOR2 gate schematic

Decoder

 


Figure 33: 4-to-16 decoder schematic

Tri-State Buffer

 


Figure 34: Tri-state buffer schematic

Tri-State Inverter

 


Figure 35: Tri-state inverter schematic

Timing of Key Signals

Memory Operation and Design Choices

Breakdown of Energy Contributions

Optimization of Energy

Validation of Correctness

Summary of Design Metrics

Honor Pledge

We, Jack Harkins and Mauricio Mutai, certify that we have complied with the University of Pennsylvania's Code of Academic Integrity in completing this project.